

이제 A & B 를 가진 flip-flop 이 있는데 만약 $A=0$ 이면 $Q^* = Q$ 이다


$A=1$ 이면 $Q^* = B$ 가 된다

a) 상태도를 그려라

b) A, B 그리고 Q 에 의한 Q^* 식 작성하라

표이


A	B	Q	Q^*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

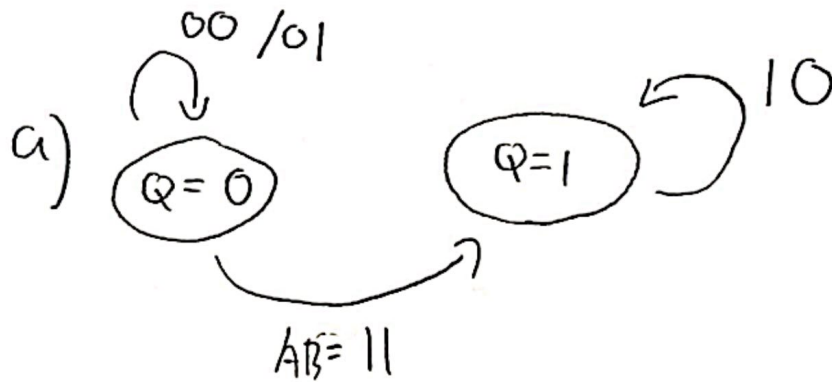

b) 논리식 $Q^* = A'Q + AB$

타이밍 플랜지

9월 14일.

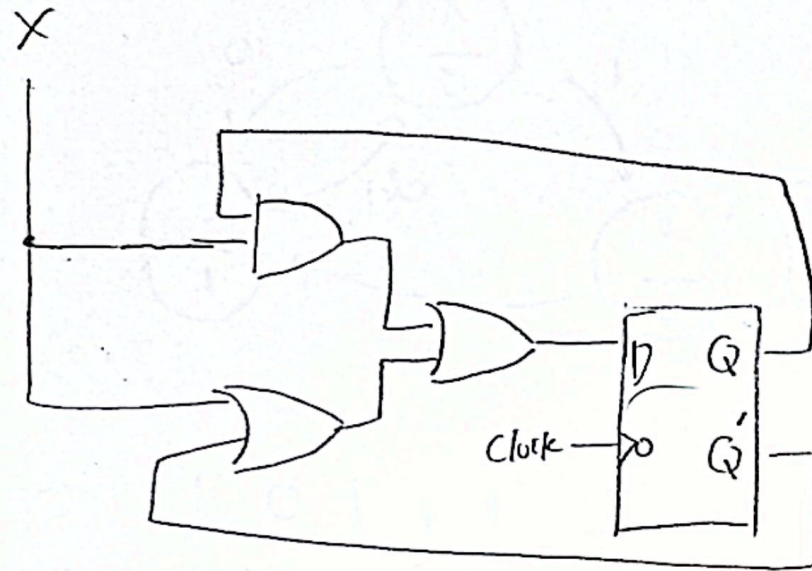

a) D flip flop


$\frac{1}{2} \times \frac{1}{2} = \frac{1}{4}$ 이다.



a) D flip flop

$$D = XQ + (Q' + X) = Q^*$$

x	Q	Q^*
0	0	1
0	1	0
1	0	1
1	1	1

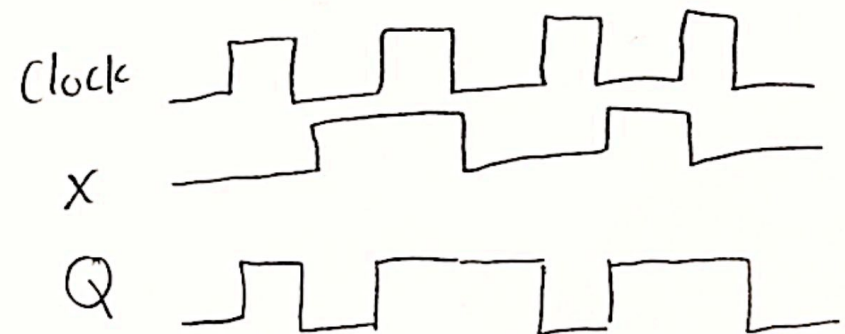

1. 다음 상태표들 각각에 대하여, 상태표와 가동할 문자를 표시하고
 완성하라


q^*

q	$x=0$	$x=1$	z
A	C	B	0
B	B	C	0
C	A	A	1

x 0 1 1 0 0 0 1

q B

z

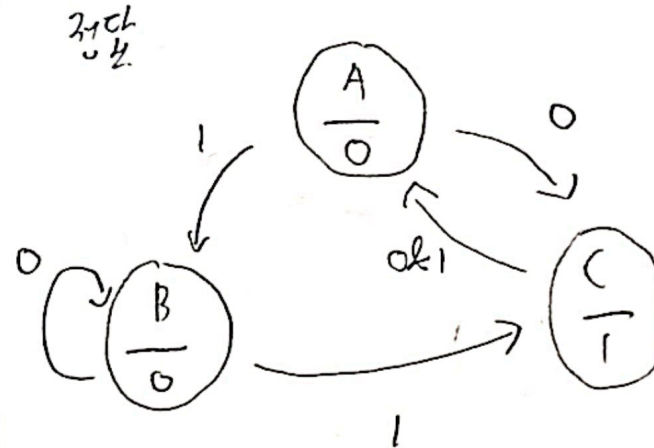

x 0 1 1 0 1 0 0 1

q B B C A B B C A C

z 0 0 1 0 0 0 1 0 1